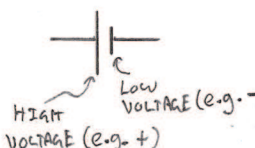
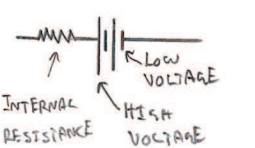

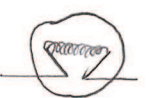

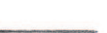
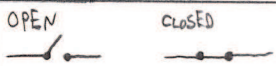
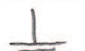


CIRCUITS


ELEMENT	SYMBOL	FUNCTION	RATING
IDEAL BATTERY		<ul style="list-style-type: none"> SUPPLY A CONSTANT SOURCE OF VOLTAGE 	<p>"ELECTROMOTIVE FORCE" $\frac{[M][L]^2}{[T]^3[A]} \equiv \mathcal{E}$</p> <p>MEASURED IN VOLTS "V"</p>
REAL BATTERY		<ul style="list-style-type: none"> SUPPLY A CONSTANT SOURCE OF VOLTAGE FOR A GIVEN CURRENT DRAW 	<ul style="list-style-type: none"> "ELECTROMOTIVE FORCE" $\equiv \mathcal{E}$ MEASURED IN VOLTS "V" WHEN NO CURRENT IS DRAWN "INTERNAL RESISTANCE" $\equiv r \approx \text{CONSTANT}$
RESISTOR		<ul style="list-style-type: none"> CONTROL AMOUNT OF CURRENT IN A CIRCUIT U^E OF CHARGE CARRIERS TRANSFORMS INTO E^{TH} OF RESISTOR 	<p>RESISTANCE $\frac{[M][L]^2}{[A]^2[T]^3} \equiv R$</p> <p>MEASURED IN OHMS "Ω"</p>
LIGHT BULB		<ul style="list-style-type: none"> PRODUCE VISIBLE LIGHT U^E OF CHARGE CARRIERS TRANSFORMS INTO $E^{TH} + E^{LIGHT}$ THE INCREASE IN TEMP OF THE FILAMENT ENSURES VISIBLE LIGHT IS EMITTED VIA THERMAL RADIATION 	<p>POWER $\frac{[M][L]^2}{[T]^3} \equiv P$</p> <p>MEASURED IN WATTS "W" AT A SPECIFIC ΔV</p> <ul style="list-style-type: none"> IDEAL LIGHT BULB ASSUME $R = \text{CONST.}$
CAPACITOR		<ul style="list-style-type: none"> STORES U^E FOR LATER USE 	<p>CAPACITANCE $\frac{[A]^2[T]^4}{[M][L]^2} \equiv C$</p> <p>MEASURED IN FARADS "F"</p> <ul style="list-style-type: none"> RATIO OF CHARGE ON 2 CONDUCTORS TO THE VOLTAGE DIFFERENCE ACROSS THEM $C = \frac{Q}{\Delta V}$
WIRE		<ul style="list-style-type: none"> PATHWAY FOR CHARGE CARRIERS TO MOVE 	<ul style="list-style-type: none"> IDEAL WIRE : $R = 0$ REAL WIRE : $R = \frac{\rho L}{A}$
SWITCH		<ul style="list-style-type: none"> MOVABLE WIRE IN CIRCUIT CONTROLLED BY USER TO COMPLETE OR BREAK A CIRCUIT 	
GROUND		<ul style="list-style-type: none"> THE COMMON CONDUCTOR IN A CIRCUIT WHERE THE CHANGE IN VOLTAGE IS REFERENCED TO RECALL THAT U^E AND V ARE ARBITRARY, ONLY CHANGES IN THEM ARE MEANINGFUL, THUS GROUND IS ANALOGOUS TO SETTING A ZERO POINT 	

CIRCUIT TOOLS

KIRCHHOFF'S VOLTAGE LOOP LAW (CONSERVATION OF ENERGY)

$\sum \Delta V_{\text{loop}} = 0$

EXAMPLE:

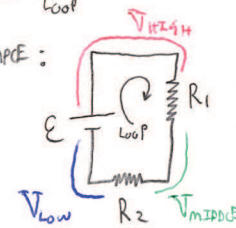


$$\Delta V_{\text{BATTERY}} + \Delta V_{R1} + \Delta V_{R2} = 0$$

$$+ \mathcal{E} - IR_1 - IR_2 = 0$$

KIRCHHOFF'S JUNCTION RULE (CONSERVATION OF CHARGE)

$\sum I_{\text{IN}} = \sum I_{\text{OUT}}$

EXAMPLE

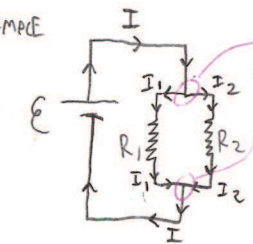

2 JUNCTIONS
BUT ONLY ONE UNIQUE EQUATION
 $I = I_1 + I_2$

OHM'S LAW

$\Delta V = IR$

POWER DISSIPATED OR SUPPLIED BY ELEMENTS IN A CIRCUIT

RESISTORS LIGHT BULBS BATTERIES

POWER = $\frac{\text{ENERGY}}{\text{TIME}} \equiv P$

RECALL $I = \frac{\Delta Q}{\Delta t}$ AND $\Delta U^E = q \Delta V$

$$I = \frac{\Delta U^E}{\Delta V \Delta t} \rightarrow \frac{\Delta U^E}{\Delta t} = I \Delta V$$

$$P = I \Delta V = \frac{\Delta V^2}{R} = I^2 R$$

USEFUL WHEN $\Delta V = \text{CONSTANT}$

USEFUL WHEN $I = \text{CONSTANT}$