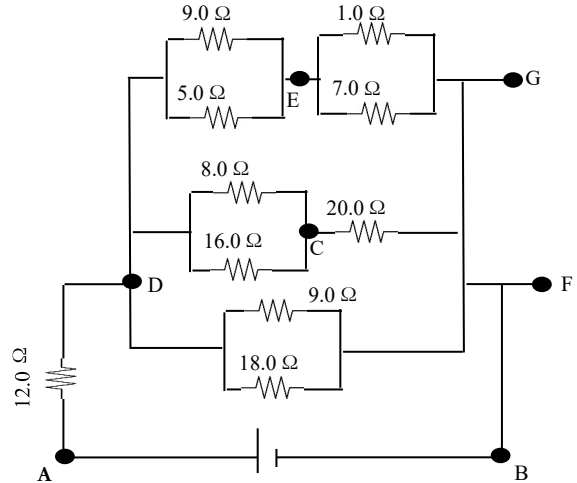


Week 8 Challenge Homework Solutions

Question 1

The current in the 8.00-Ω resistor in the drawing is 0.500 A.


- Find the current in the 20.0-Ω, 12.0-Ω, and both 9.0Ω resistors.
- Find the voltage drop and indicate which point is at a higher potential for following: between points **G** and **F**, **A** and **B**, **A** and **E**, and **E** and **C**.
- A brand new standard household 9-V battery has about the same potential energy as a 2200 lb car at the top of a 1200-ft-high hill. How long will the circuit operate if its voltage source is replaced with a 9-V battery?



$$(a) \quad I_8 = 0.5 \text{ A} \Rightarrow \Delta V_8 = 4 \text{ V} \Rightarrow \Delta V_{16} = 4 \text{ V} \Rightarrow I_{16} = 0.25 \text{ A}$$

$$I_{20} = I_8 + I_{16} = \boxed{0.75 \text{ A} = I_{20}} \Rightarrow \Delta V_{20} = 15 \text{ V} \Rightarrow \Delta V_{DF} = 19 \text{ V}$$
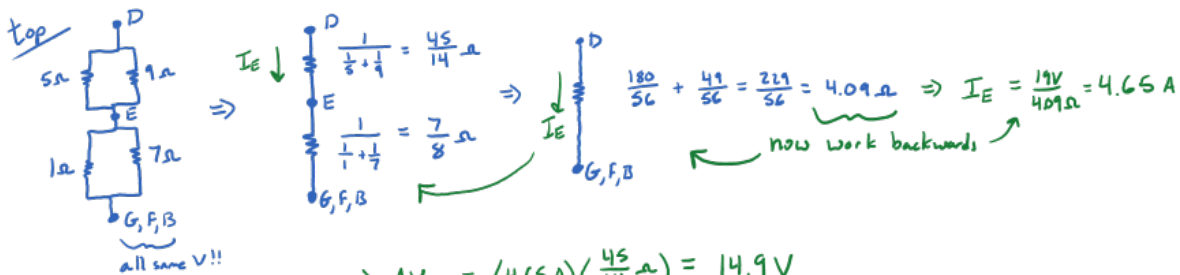
$$\Rightarrow \Delta V_{9_{bot}} = 19 \text{ V} \Rightarrow \Delta I_{9_{bot}} = \frac{19}{9} \text{ A} = 2.11 \text{ A} \Rightarrow I_{18} = \frac{1}{2} I_{9_{bot}} = 1.06 \text{ A}$$



$$\Rightarrow \Delta V_{DE} = (4.65 \text{ A}) \left(\frac{45}{14} \Omega \right) = 14.9 \text{ V}$$

$$\Delta V_{9_{top}} = 14.9 \text{ V}$$

$$\Rightarrow I_{9_{top}} = \frac{14.9 \text{ V}}{9 \Omega} = 1.66 \text{ A}$$

$$\Delta V_{12} = 102.8 \text{ V}$$

$$I_E = I_{9_{top}} + I_8 \Rightarrow I_{12} = I_{18} + I_{9_{bot}} + I_{20} + I_E = \boxed{8.57 \text{ A} = I_{12}}$$

(b) G → F

A → B

$$\Delta V = 0 \text{ V} \quad -\Delta V_{BA} = \Delta V_{AB} = \Delta V_{R_2} + \Delta V_{q_{\text{bot}}}$$

$$V_A > V_B$$

$$V_G = V_F$$

$$= -122 \text{ V}$$

A → E

$$V_A > V_E$$

E → C

$$V_C > V_E$$

$$\Delta V_{AE} = \Delta V_{R_2} + \Delta V_{q_{\text{top}}}$$

$$= 118 \text{ V}$$

$$\Delta V_{EC} = -\Delta V_{q_{\text{top}}} + \Delta V_{R_8}$$

$$= 10.9 \text{ V}$$

(c)

$$U_{\text{car}}^g = mgh = (2200 \text{ lb})(9.8 \text{ m/s}^2)(1200 \text{ ft})$$

$$\times \left(\frac{1 \text{ kg}}{2.2 \text{ lb}} \right) \left(\frac{1 \text{ m}}{3.30 \text{ ft}} \right)$$

$$= 3.56 \times 10^6 \text{ J}$$

$$R_{\text{circuit}} = \frac{\Delta V_{BA}}{I_{\text{cir}}} = \frac{122 \text{ V}}{8.57 \text{ A}} = 14.2 \Omega$$

↑
 I_{R_2}

$$P = \frac{\Delta V^2}{R} = \frac{(9 \text{ V})^2}{14.2 \Omega} = 5.70 \text{ W}$$

$$P = \frac{\Delta U}{\Delta t} \Rightarrow \Delta t = \frac{\Delta U}{P} = \frac{3.56 \times 10^6 \text{ J}}{5.70 \text{ J/s}} = 6.25 \times 10^5 \text{ s}$$

$$= 10,400 \text{ min} = 173 \text{ hr} = 7.2 \text{ days}$$