

W8. DC Circuits


- Resistance
- Ohm's law
- Power
- Kirchhoff's law
- Equivalent circuit

Resistance





$$R = \rho \frac{L}{A}$$

$$\sigma = \frac{1}{\rho}$$


conductivity

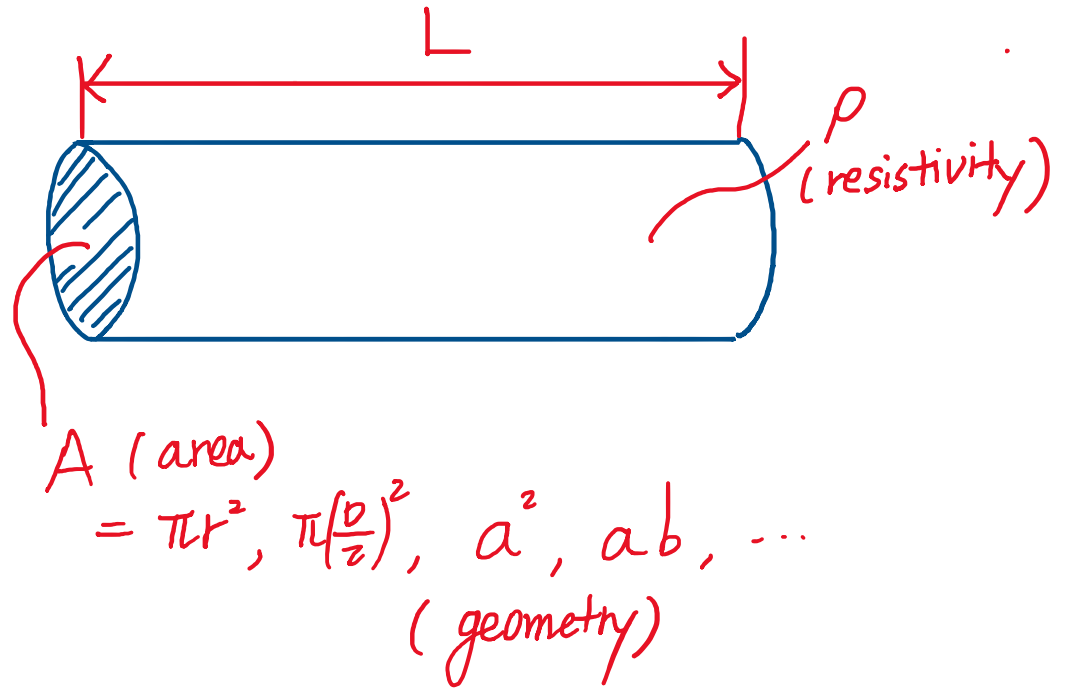

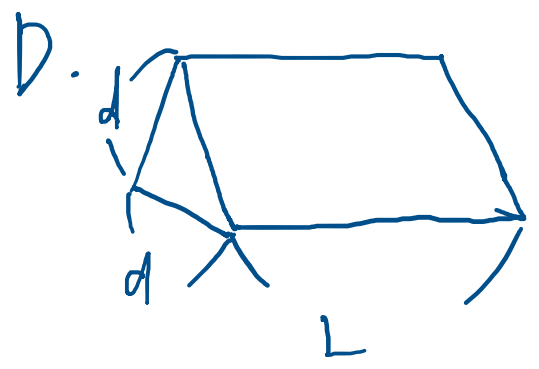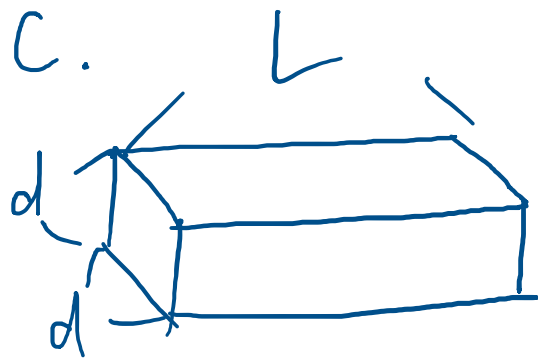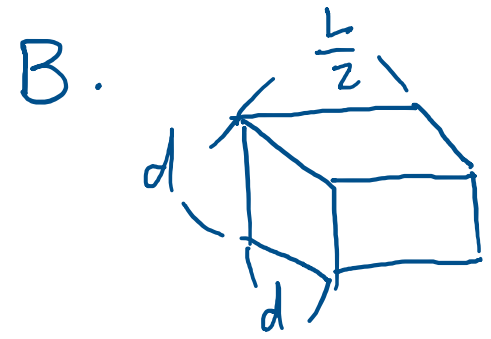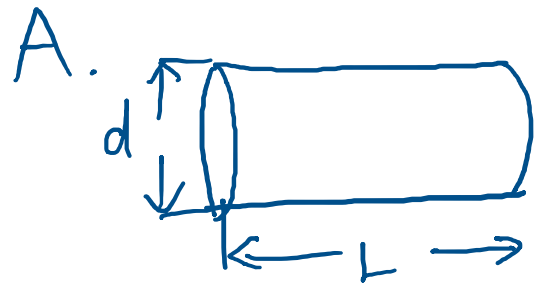Four resistors are made out of the same materials. Rank the resistors A, B, C, and D from least to greatest resistance




A.

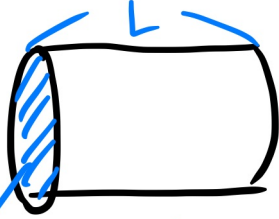

$$A = \left(\frac{D}{2}\right)^2 \pi$$

$$R_A = \frac{\rho L}{\left(\frac{\pi D^2}{4}\right)} = \frac{4}{\pi} \frac{\rho L}{D^2}$$


B.

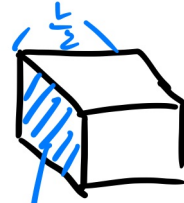

$$A = d^2$$

$$R_B = \frac{\rho \frac{L}{2}}{d^2} = \frac{1}{2} \frac{\rho L}{d^2}$$

C.

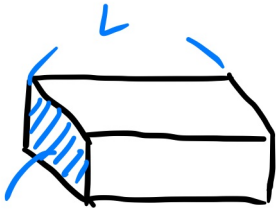


$$A = d^2$$

$$R_C = \frac{\rho L}{d^2}$$



D.

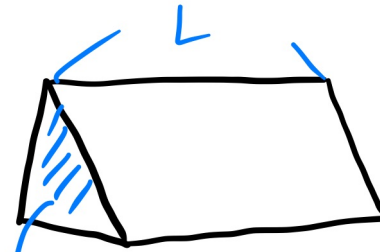


$$A = d \left(\frac{\sqrt{3}}{2}d\right) \frac{1}{2} = \frac{\sqrt{3}}{4} d^2$$

$$R_D = \frac{\rho L}{\frac{\sqrt{3}}{4} d^2} = \frac{4}{\sqrt{3}} \frac{\rho L}{d^2}$$

$$\Rightarrow B < C < A < D$$

Ohm's law & power

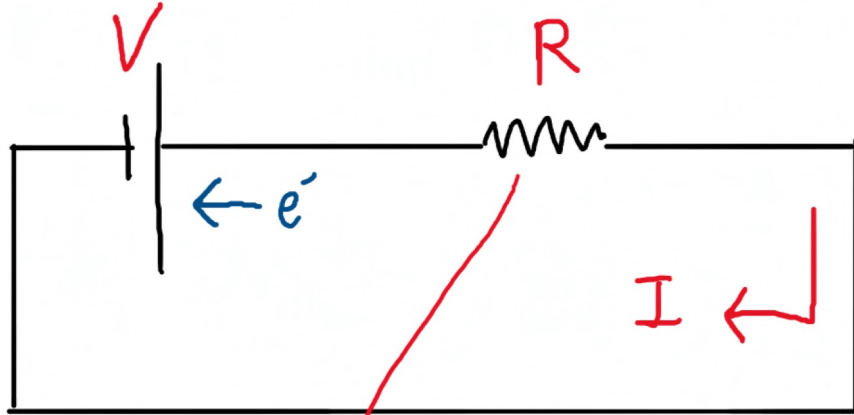

$$\left[\begin{array}{l} I = \frac{V}{R} \\ V = IR \\ R = \frac{V}{I} \end{array} \right] \quad I = \frac{\Delta q}{\Delta t}$$




$$\text{Power} = IV \rightarrow$$

$$I_{\text{@ element}} \quad V_{\text{@ element}}$$

$$= \frac{V^2}{R}$$

$$= I^2 R$$

< Series >

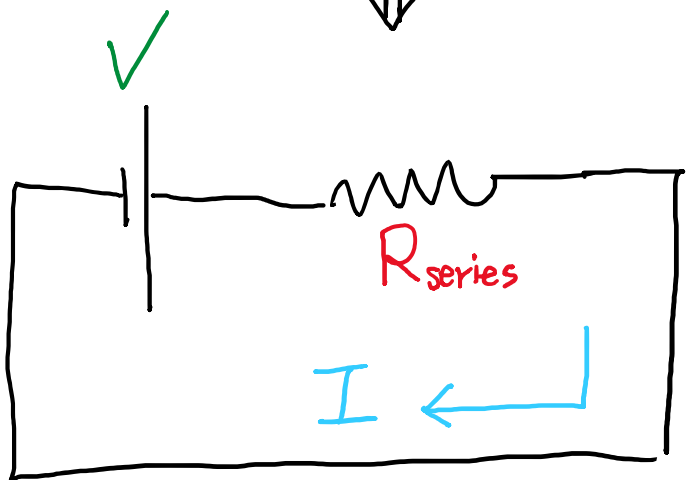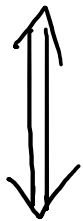
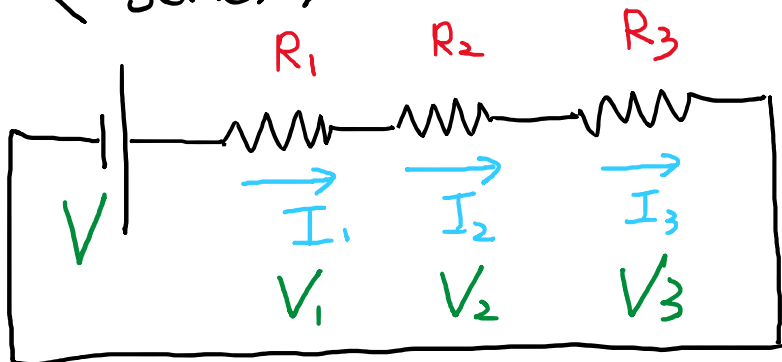


$$R_{series} = R_1 + R_2 + R_3$$

$$I_{series} = I_1 = I_2 = I_3$$

$$V_{series} = V_1 + V_2 + V_3$$


< Parallel >

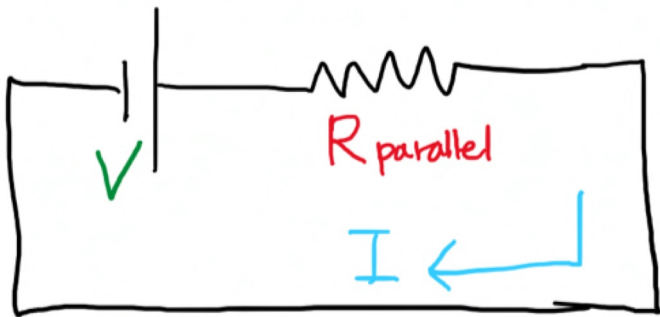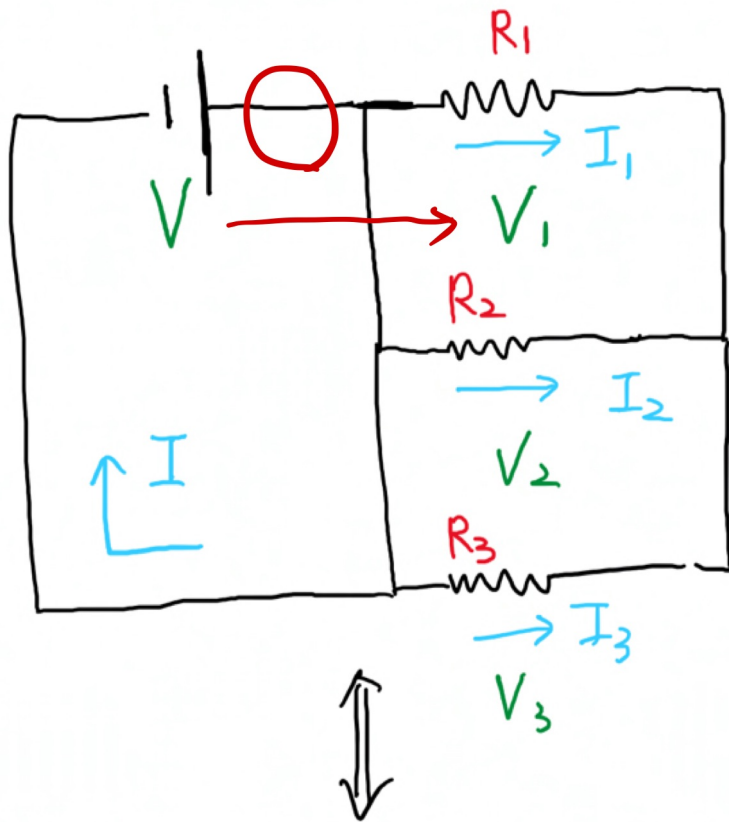

$$R_{\text{parallel}} = \left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right]^{-1}$$


$$I_{\text{parallel}} = I_1 + I_2 + I_3$$
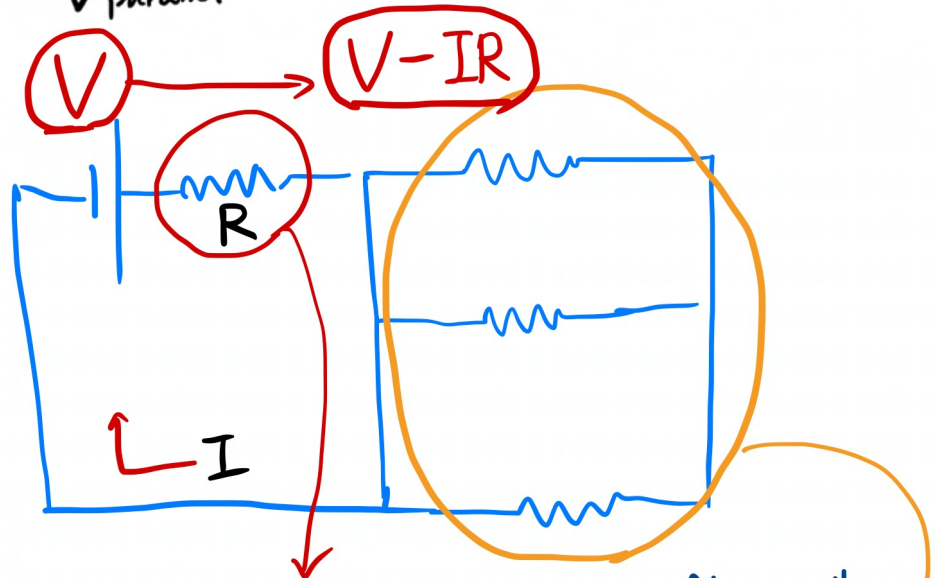
$$V_{\text{parallel}} = V_1 = V_2 = V_3$$



Voltage drops by IR after the element.

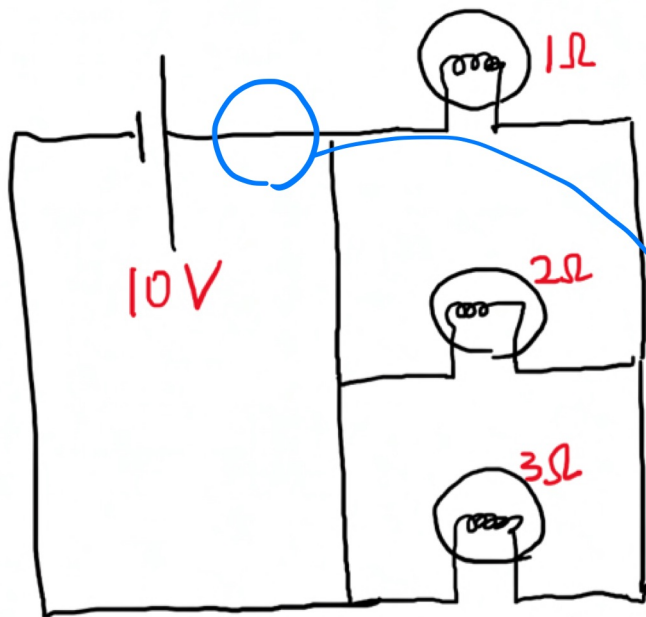Voltage across on parallel elements would be $(V-IR)$



⇒ Parallel connection

$$V = V_1 = V_2 = V_3$$

$$\hookrightarrow P = \frac{V^2}{R}$$

No element → There is not a voltage drop from the source.

↓

$$V = 10V = V_1 = V_2 = V_3$$

Rank from brightest to dimmest.

$$P_1 = \frac{(10V)^2}{1\Omega} = 100W$$

$$P_2 = \frac{(10V)^2}{2\Omega} = 50W$$

$$P_3 = \frac{(10V)^2}{3\Omega} = 33.3W$$


brightest

dimmest.

$1\Omega - 2\Omega - 3\Omega$


Kirchhoff's rule

- Junction rule



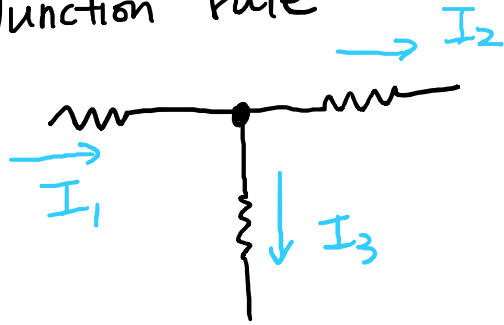


$$\Rightarrow I_1 = I_2 + I_3$$

- Loop rule

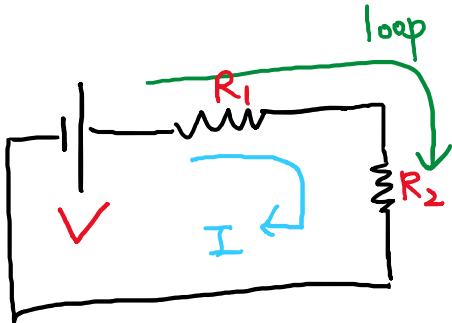
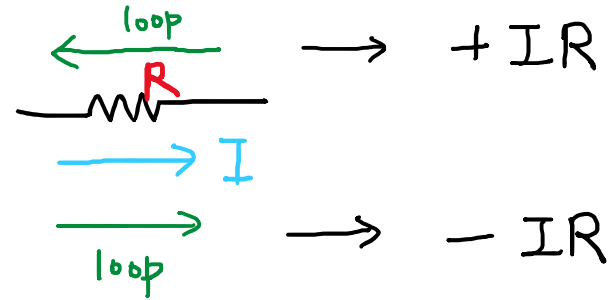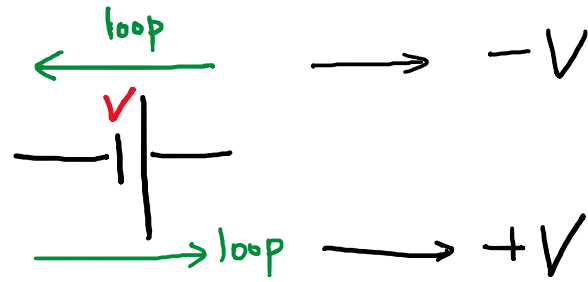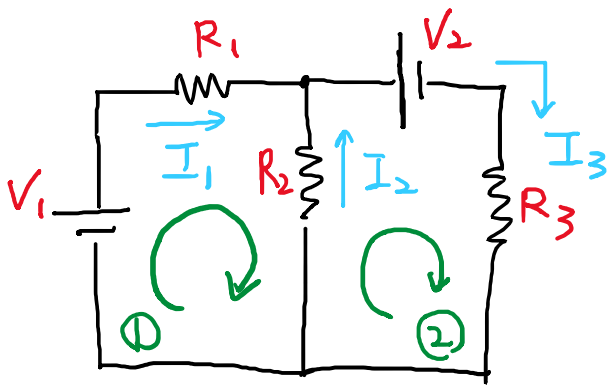
$$\Rightarrow \sum V_{\text{loop}} = V - IR_1 - IR_2 = 0$$




①

$$+V_1 - I_1 R_1 + I_2 R_2 = 0$$

②

$$-I_2 R_2 - V_2 - I_3 R_3 = 0$$

$$\textcircled{+} I_1 + I_2 = I_3$$

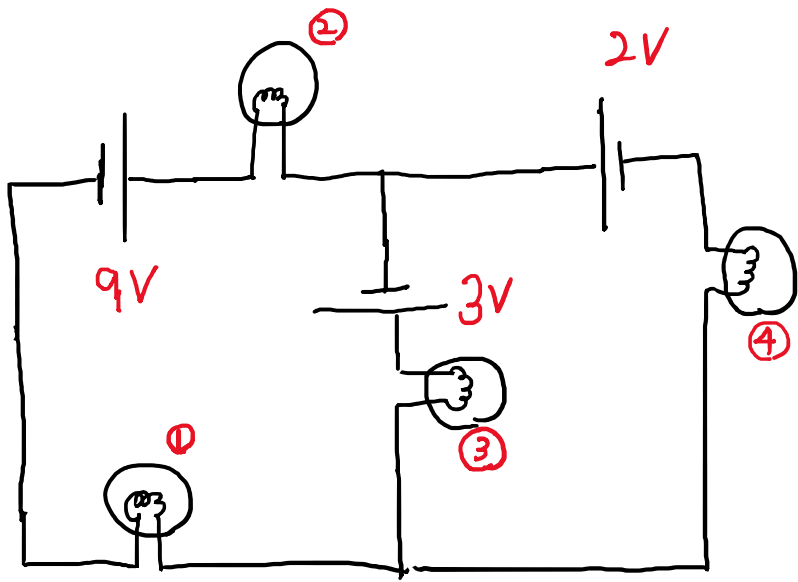

Identical light bulbs with resistance 2Ω . Rank from the brightest to dimmest.