
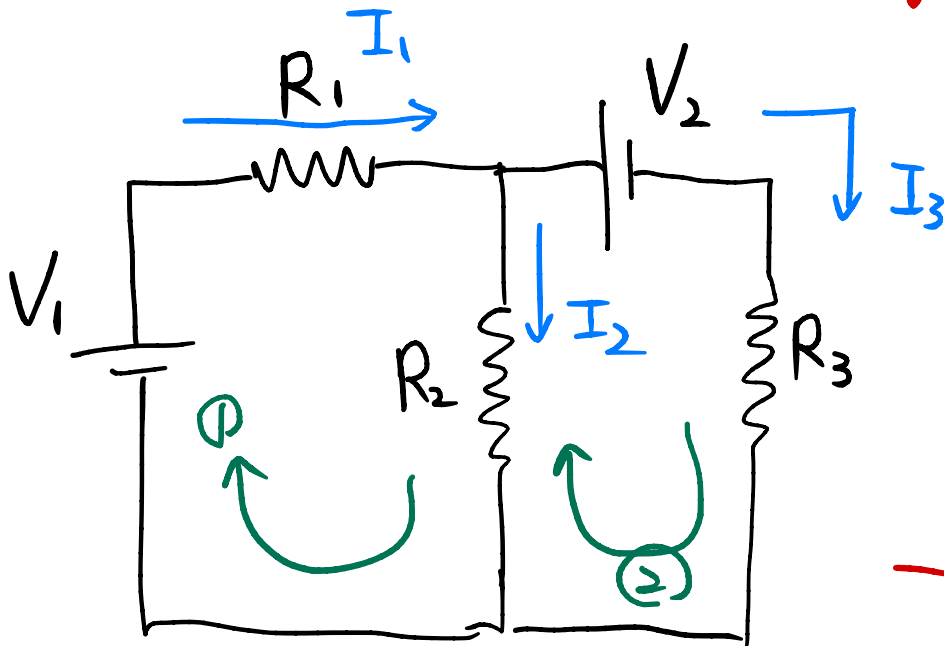
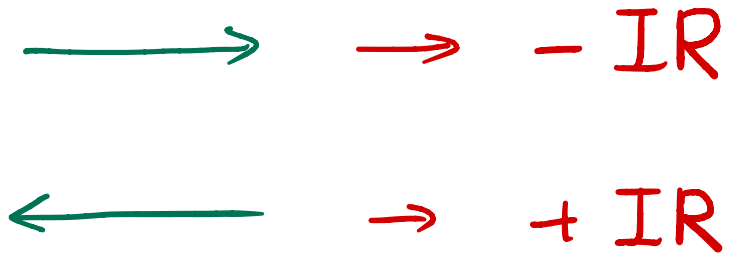
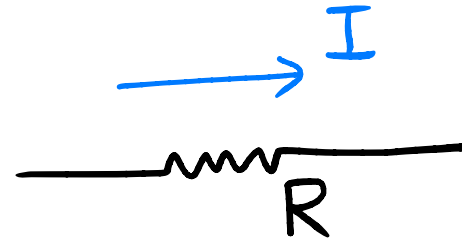
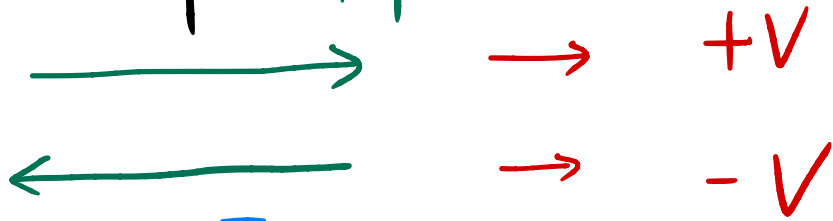


## W 9.

- Kirchhoff's law
- Equivalent circuit.
- Magnetic field?

# < Kirchhoff's law >

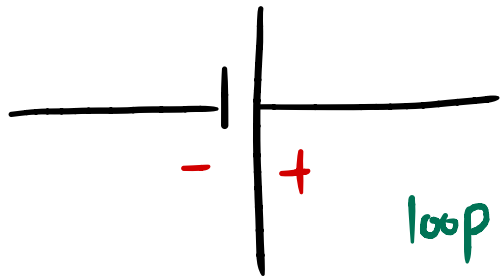

- Junction rule  
 $\sum I_{in} = \sum I_{out}$


$$I_1 = I_2 + I_3$$

$$\textcircled{1} V_1 - I_1 R_1 - I_2 R_2 = 0$$

$$\textcircled{2} +I_2 R_2 - V_2 - I_3 R_3 = 0$$
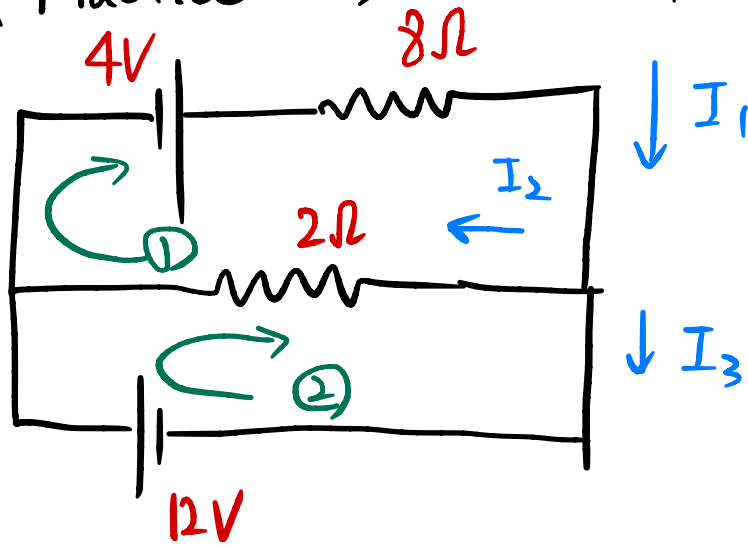
# < Practice 1 >

Find the current in the  $8\Omega$  and  $2\Omega$  resistors.



$$\left[ \begin{array}{l} \bullet \quad I_1 = I_2 + I_3 \\ \textcircled{1} \quad 4V - 8I_1 - 2I_2 = 0 \\ \textcircled{2} \quad 2I_2 + 12V = 0 \end{array} \right.$$

$$\Rightarrow 2I_2 + 12V = 0$$

$$\underline{I_2 = -6A}$$


$$4V - 8I_1 - 2I_2 = 0$$

$$4V - 8I_1 - 2(-6) = 0$$

$$\underline{I_1 = 2A}$$
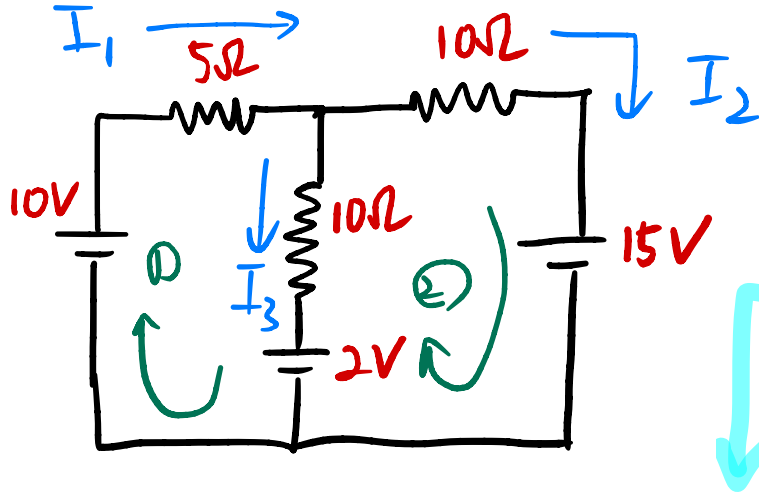
# < Practice 2 >

Determine the voltage across  $5\Omega$  resistor.



$$I_1 = I_2 + I_3$$

$$\textcircled{1} 10V - 5I_1 - 10I_3 - 2 = 0$$

$$\textcircled{2} 2V + 10I_3 - 10I_2 - 15 = 0$$

$$I_1 = I_2 + I_3 \longrightarrow$$

$$I_2 = I_1 - I_3$$

$$10I_3 - 10I_2 - 13 = 0 \longrightarrow$$

$$10I_3 - 10(I_1 - I_3) - 13 = 0$$

$$20I_3 = 10I_1 + 13$$

$$I_3 = 0.5I_1 + 0.65$$

$$10 - 5I_1 - 10(0.5I_1 + 0.65) = 0$$

$$10 - 10I_1 - 6.5 = 0$$


$$I_1 = 0.15A.$$

$$\Delta V_{5\Omega} = 5\Omega \cdot (0.15A)$$

$$= 0.75V$$

# < Challenge HW >

Wheatstone bridge.

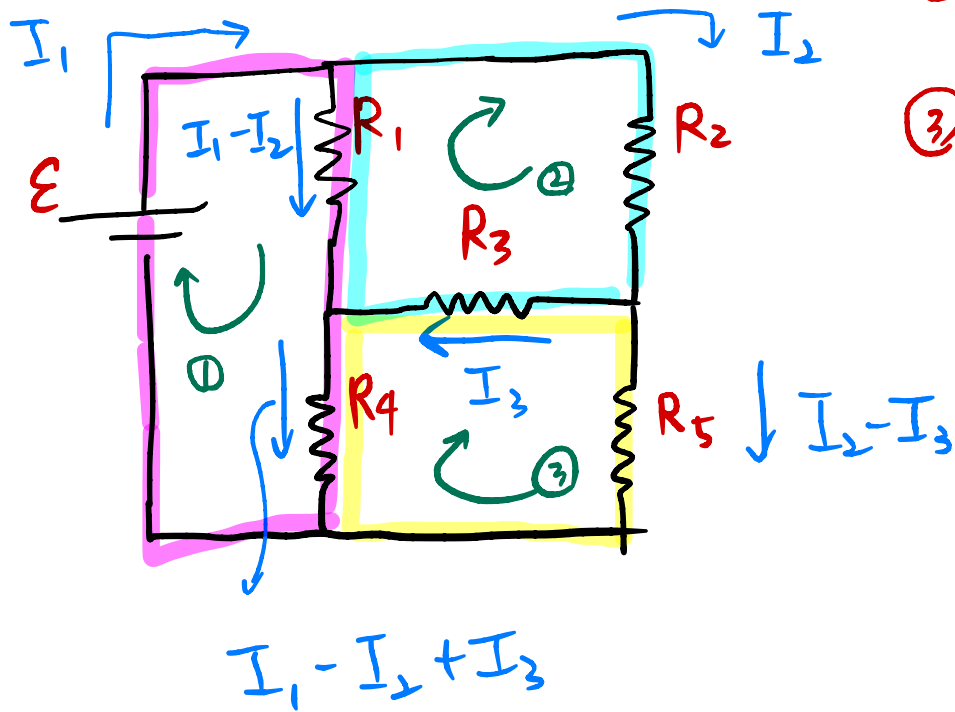


$$\textcircled{1} \quad \mathcal{E} - R_1 (I_1 - I_2) - R_4 (I_1 - I_2 + I_3) = 0$$
$$\textcircled{2} \quad R_1 (I_1 - I_2) - R_2 I_2 - R_3 I_3 = 0$$
$$\textcircled{3} \quad R_3 I_3 - R_5 (I_2 - I_3) + R_4 (I_1 - I_2 + I_3) = 0$$

# < Practice 3 >



Find the equivalent resistance between A and B




$R = 16 + 8 = 24\Omega$

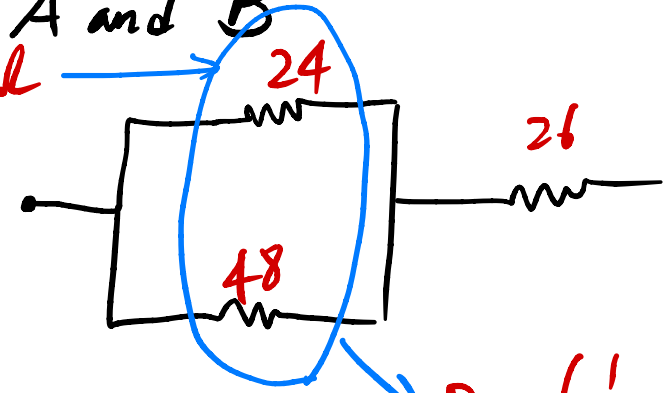


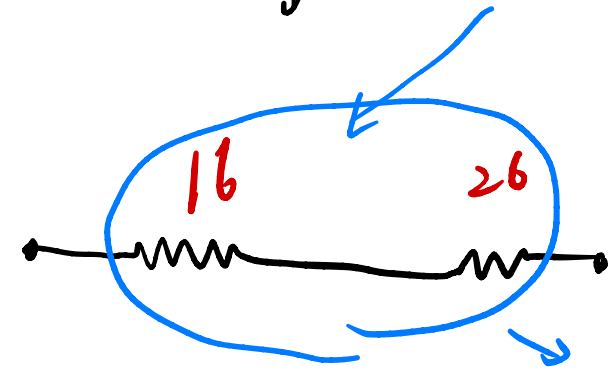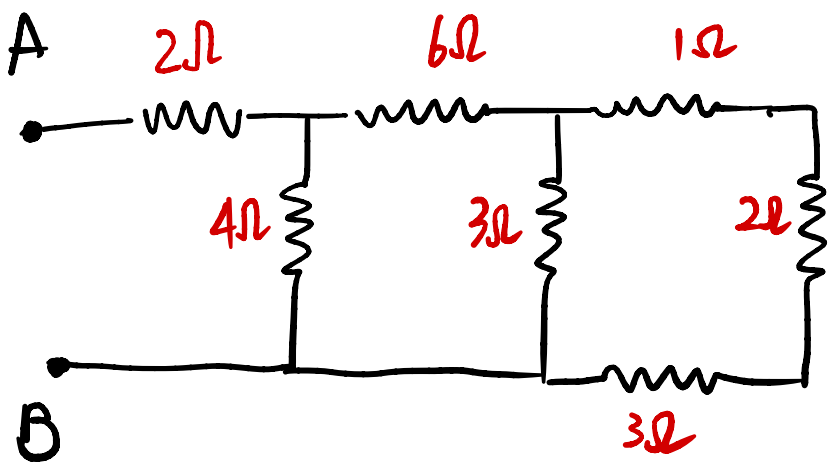$R = \left(\frac{1}{24} + \frac{1}{48}\right)^{-1} = 16$




$R = 16 + 21 = 42$

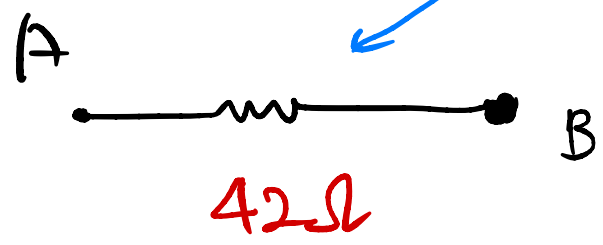


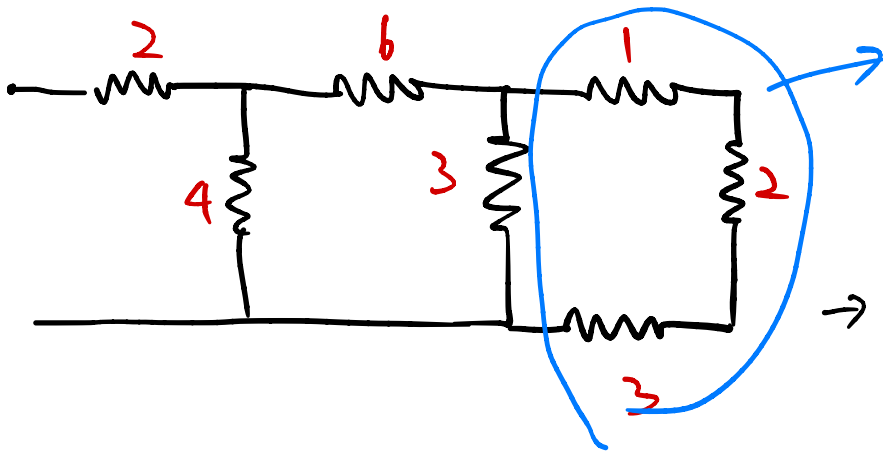

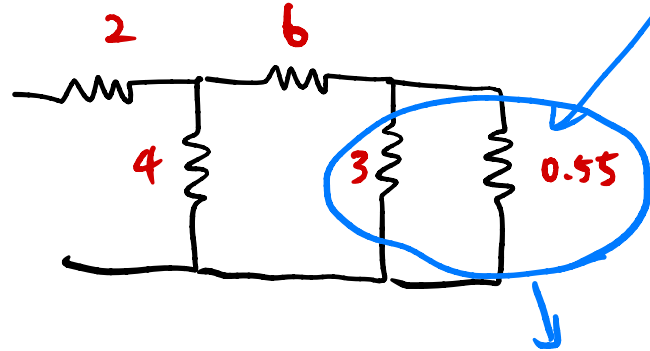
$$R = \left(1 + \frac{1}{2} + \frac{1}{3}\right)^{-1} = 0.55\Omega$$



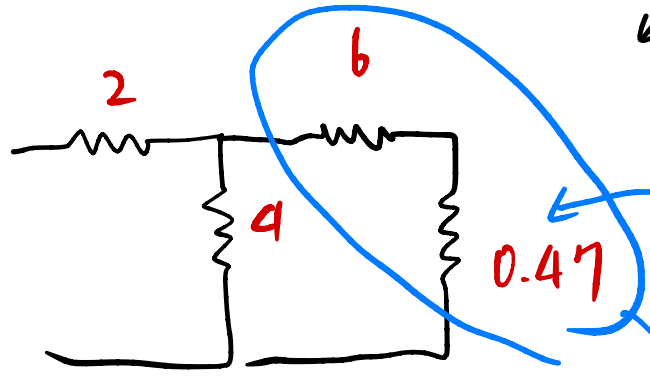
$$R = \left(\frac{1}{3} + \frac{1}{0.55}\right)^{-1} = 0.47\Omega$$



$$R = 6 + 0.47 = 6.47\Omega$$

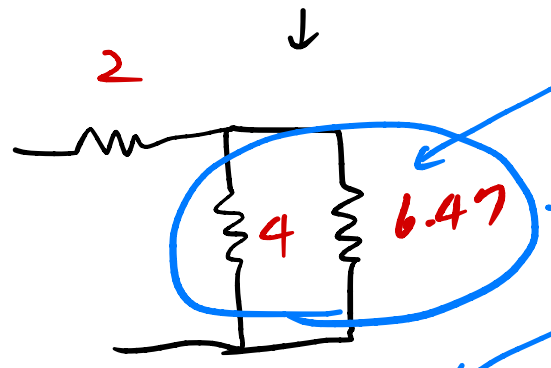

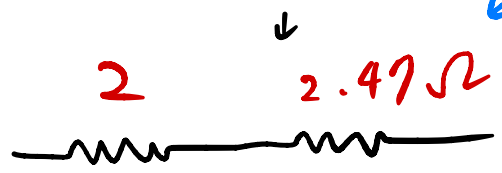
$$R = \left(\frac{1}{4} + \frac{1}{6.47}\right)^{-1} = 2.47\Omega$$



$$4.47\Omega$$



# < Practice 4 >

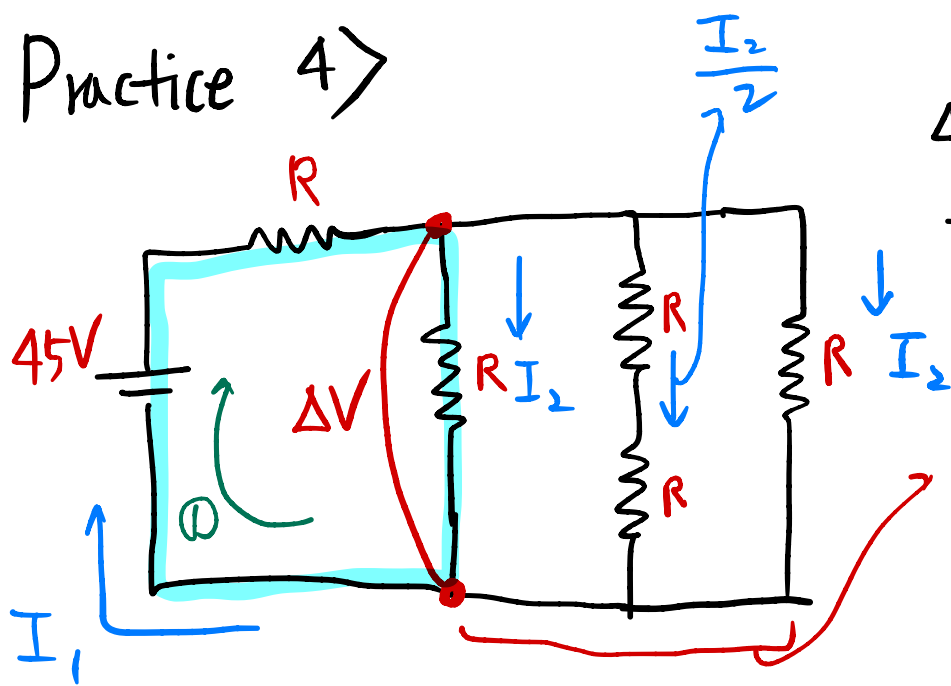

45V battery delivers 58W of power to the circuit. What is the resistance R?

Parallel → have the same voltage ( $\Delta V$ )

$$\Delta V = 45 - RI_1 \quad \downarrow$$

Let current on single R be  $I_2$ .

Then, current on  $2R$  is  $\frac{I_2}{2}$ .

Junction rule

$$I_1 = I_2 + \frac{I_2}{2} + I_2 = \frac{5}{2} I_2$$

$$\textcircled{1} 45 - RI_1 - RI_2 = 0$$

$$45 - R\left(\frac{5}{2}I_2\right) - RI_2 = 0 \rightarrow \frac{7}{2}RI_2 = 45$$

$$I_2 = \frac{90}{7R}$$

$$I_1 = \frac{5}{2} \left( \frac{90}{7R} \right) = \frac{225}{7R}$$

Total power




$$P = I_1^2 R + I_2^2 R + 2R \left( \frac{I_2}{2} \right)^2 + I_2^2 R$$

$$= I_1^2 R + \frac{5}{2} I_2^2 R$$

$$= \left( \frac{225}{7R} \right)^2 R + \frac{5}{2} \left( \frac{90}{7R} \right)^2 R = \frac{1446.4}{R} = 58 \text{ W}$$

$$\Rightarrow R = \underline{25 \Omega}$$

# < Magnetic field >

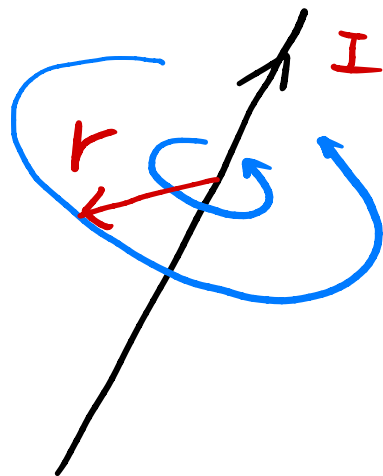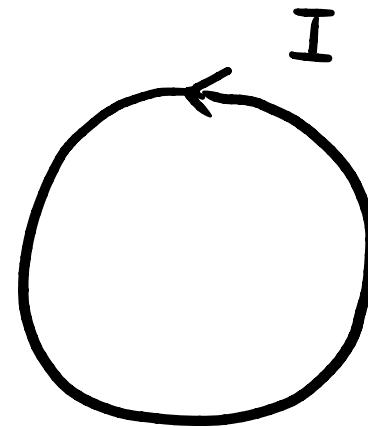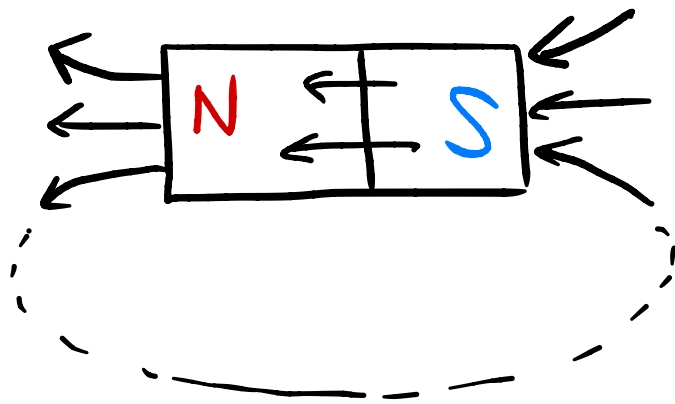

$$B = \frac{\mu_0 I}{2\pi r}$$

